

Experiment 1 - Clock and Periodic Signal Generation

Bitra Nasiri Zarandi

810199504

Ali Padyav

810199388

Abstract— In This report we explain about our activities for experiment 1 in DLD lab and it's related to clock generation.

Keywords— LM555, Ring Oscillator, Schmitt Trigger Oscillator, Frequency Divider, T Flip-Flop.

1. Clock Generation using ICs and Analog components.

1.1 Ring Oscillator

1. The circuit that we made:

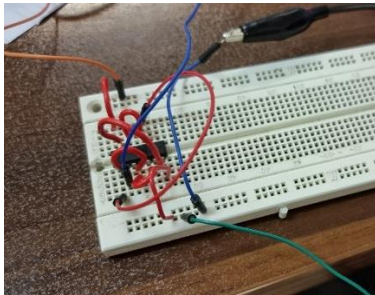


Fig. 1 Ring oscillator circuit

Result of circuit:

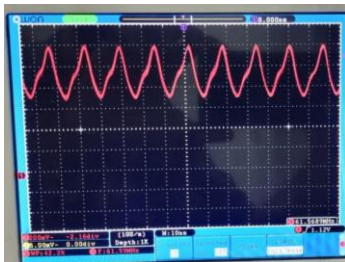


Fig. 2 Ring oscillator waveform

$$f = 61.59 \text{ MHz} \Rightarrow T_{\text{delay}} = 1/f = 16.23 \text{ ns}$$

$$2. N = 5$$

$$T_{\text{delay}} = 2N \cdot T_{\text{Inv}} \Rightarrow 16.23 = 10 \cdot T_{\text{Inv}} \Rightarrow T_{\text{Inv}} = 1.623 \text{ ns}$$

1.2 LM555 timer

1. The circuit:

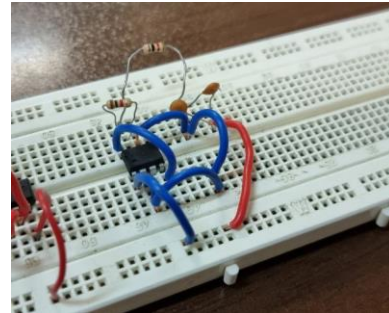


Fig. 3 LM555 circuit

Oscillator Result for $R = 50 \text{ K}\Omega$:



Fig. 4 wave of 50KΩ circuit

$$f = 1.206 \text{ KHz} , \text{ Duty Cycle} = 49.3\%$$

2. Oscillator Result for $R_2 = 100 \text{ K}\Omega$:



Fig. 5 wave of 100KΩ circuit

Experiment 1 - Clock and Periodic Signal Generation

Bitra Nasiri Zarandi

810199504

Ali Padyav

810199388

$f = 618.8 \text{ Hz}$, Duty Cycle = 49.3%

calculation values:

$R_2 = 100\text{K}\Omega$

$T = 0.693(2R_2 + R_1)C \Rightarrow T = 1.393 \text{ ms}$

$\Rightarrow f = 1/(1.393\text{ms}) = 717.87 \text{ Hz}$

Duty Cycle = $(R_2 + R_1) / (2R_2 + R_1)$

$\Rightarrow \text{Duty Cycle} = 101/201 = 0.502 = 50.2 \%$

Oscillator Result for $R_2 = 10\text{K}\Omega$:



Fig. 6 wave of $10\text{K}\Omega$ circuit

$f = 5.806 \text{ KHz}$, Duty Cycle = 51.2%

calculation values:

$R_2 = 10\text{K}\Omega$

$T = 0.693(2R_2 + R_1)C \Rightarrow T = 145.53\mu\text{s}$

$\Rightarrow f = 1/(145.53\mu\text{s}) = 6.871 \text{ KHz}$

Duty Cycle = $(R_2 + R_1) / (2R_2 + R_1)$

$\Rightarrow \text{Duty Cycle} = 11/21 = 0.523 = 52.3 \%$

Oscillator Result for $R_2 = 1\text{K}\Omega$:



Fig. 7 wave of $1\text{K}\Omega$ circuit

$f = 36.83 \text{ KHz}$, Duty Cycle = 62.9%

calculation values:

$R_2 = 1\text{K}\Omega$

$T = 0.693(2R_2 + R_1)C \Rightarrow T = 20.79 \mu\text{s}$

$\Rightarrow f = 1/(20.79\mu\text{s}) = 48.1 \text{ KHz}$

Duty Cycle = $(R_2 + R_1) / (2R_2 + R_1)$

$\Rightarrow \text{Duty Cycle} = 2/3 = 0.666 = 66.6 \%$

As we can see in calculations, our results are close to the clock signal we see on the output and the formula is a good approximate.

1.3 Schmitt Trigger Oscillator

1. The circuit:

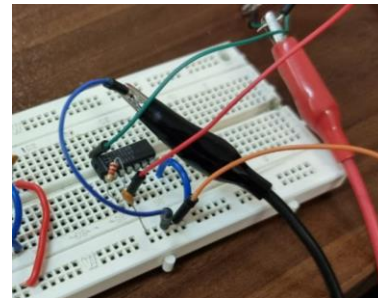


Fig. 8 Schmitt inverter oscillator circuit

$R = 2200 \Omega$:

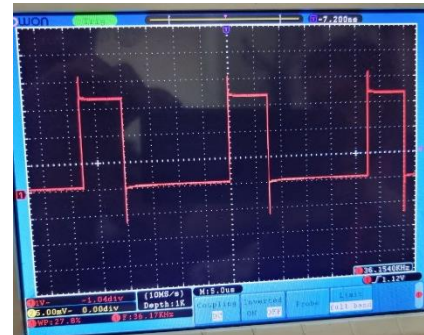


Fig. 9 wave of 2200Ω circuit

$f = 36.17 \text{ KHz}$

Experiment 1 - Clock and Periodic Signal Generation

Bitra Nasiri Zarandi

810199504

Ali Padyav

810199388

$R = 470 \Omega$:



Fig. 10 wave of 470Ω circuit

$f = 165.6 \text{ KHz}$

$R = 1 \text{ K}\Omega$:



Fig. 11 wave of 1000Ω circuit

$f = 79.62 \text{ KHz}$

2. Finding α

$$f = \alpha / RC, C = 10\text{nF}$$

$$R = 2200\Omega \Rightarrow \alpha = 0.79574$$

$$R = 470\Omega \Rightarrow \alpha = 0.77832$$

$$R = 1000\Omega \Rightarrow \alpha = 0.7962$$

As we can see results of calculating α parameter are close to each other and all of them are close to 0.79 .

1.4 Synchronous Counter as a Frequency Divider

1. We used part 1.1 circuit and generate a clock signal which you can see here

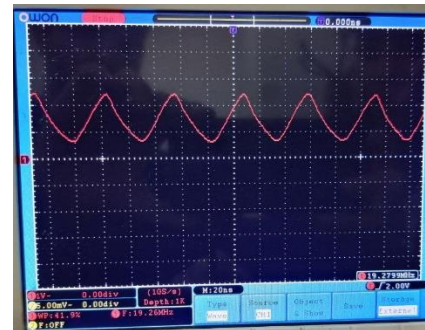


Fig. 12 clock signal from part 1

2. As you can see we closed the circuit, by using 74HC08 as a AND gate. According to the sheet and based on what value we want to divide (divide by 200) , we initialized 56 (256 – 200) With Vcc and Gnd .

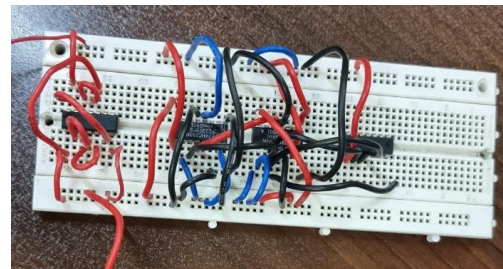


Fig. 13 Frequency divider circuit

3. We can see the result here

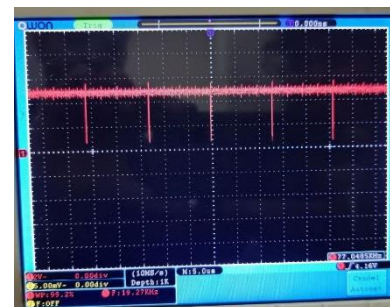


Fig. 14 output waveform

Experiment 1 - Clock and Periodic Signal Generation

Bita Nasiri Zarandi

810199504

Ali Padyav

810199388

F = 19.27 KHz

1.5 T Flip-Flop

Add a T Flip-Flop to circuit

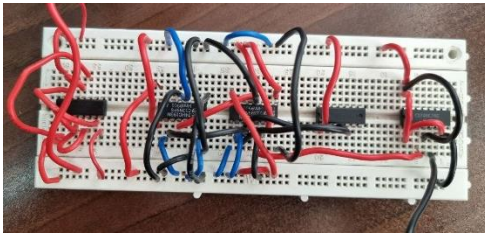


Fig. 15 T Flip-Flop circuit

Now we can see the result



Fig. 16 T Flip-Flop waveform

As we can see 50% duty cycle has been produced after adding T Flip-Flop.