

Experiment 3 - Function Generator

Ali Padyav, 810199388

Bitra Nasiri, 810199504

Abstract— This document is a report about designing Function Generator and implementing on FPGA for the 3rd experiment of the DLD Lab (ECE 045) at University of Tehran, Department of Electrical and Computer Engineering.

Keywords— Function Generator, PWM, DAC, FPGA Programming, Altera Cyclone II, Quartus, RTL Design

I. WAVEFORM GENERATOR

A. Code of Waveform Generator

```
1 module sine_wave(input clk, rst, output [7:0] sin);
2   reg signed [15:0] sin_t = 16'd0, cos_t = 16'd30000;
3   reg signed [15:0] sin_r, cos_r;
4
5   always @(posedge clk)
6   begin
7     if (rst)
8     begin
9       sin_t = 16'd0;
10      cos_t = 16'd30000;
11    end
12    else
13    begin
14      sin_r = sin_t + (cos_t >>> 6);
15      cos_r = cos_t - (sin_r >>> 6);
16      sin_t = sin_r;
17      cos_t = cos_r;
18    end
19  end
20
21  assign sin = sin_r[15:8] + 8'd127;
22 endmodule
```

Fig. 1 Verilog description of sine wave

```
1 module half_wave(input [7:0] sine, output reg [7:0] out);
2   always @(sine)
3   begin
4     if (sine < 8'd128)
5       out = 8'd127;
6     else
7       out = sine;
8   end
9 endmodule
```

Fig. 2 Verilog description of half wave

```
1 module full_wave(input [7:0] sine, output reg [7:0] out);
2   always @(sine)
3   begin
4     if (sine < 8'd128)
5       out = 8'd255 - sine;
6     else
7       out = sine;
8   end
9 endmodule
```

Fig. 3 Verilog description of full wave

```
1 module square_wave(input clk, rst, output reg [7:0] square);
2   reg [7:0] count = 8'd0;
3
4   always @(posedge clk)
5   begin
6     if (rst)
7       count = 8'd0;
8     else
9       count = count + 1;
10
11     if (count < 128)
12       square = 8'd0;
13     else
14       square = 8'd255;
15   end
16 endmodule
```

Fig. 4 Verilog description of square wave

```
1 module triangle_wave(input clk, rst, output reg [7:0] triangle);
2   reg [7:0] count = 8'd0;
3
4   always @(posedge clk)
5   begin
6     if (rst)
7     begin
8       triangle <= 8'b0;
9       count <= 1'b0;
10    end
11    else
12    begin
13      count <= count + 1'b1;
14      if (count < 8'd127)
15        triangle <= triangle + 2'd2;
16      else if (count == 8'd 127)
17        triangle <= triangle + 2'd1;
18      else if (count == 8'd255)
19        triangle <= triangle - 2'd1;
20      else
21        triangle <= triangle - 2'd2;
22    end
23  end
24 endmodule
```

Fig. 5 Verilog description of triangle wave

```

1 module reciprocal_wave(input clk, rst, output reg [7:0] out);
2     reg [7:0] count = 8'd0;
3
4     always @(posedge clk)
5     begin
6         out <= 8'b0;
7         if (rst)
8             begin
9                 out <= 8'b0;
10                count <= 1'b0;
11            end
12        else
13            begin
14                count <= count + 1'b1;
15                if (count >= 8'd252)
16                    out <= 8'd4;
17                else
18                    out <= 8'd255 / (8'd63 - (count >> 2));
19            end
20        end
21    endmodule

```

Fig. 6 Verilog description of reciprocal wave

```

1 module wave_generator(input clk, rst, output[7:0] reciprocal, square,
2                       triangle, sine, half_wave, full_wave);
3
4     reciprocal_wave rw1(clk, rst, reciprocal);
5     square_wave sqwave_w1(clk, rst, square);
6     triangle_wave tw1(clk, rst, triangle);
7     sine_wave sine_w1(clk, rst, sine);
8     half_wave hw1(sine, half_wave);
9     full_wave fw1(sine, full_wave);
10 endmodule

```

Fig. 6 Verilog description of whole waveform generator

B. Block Diagram

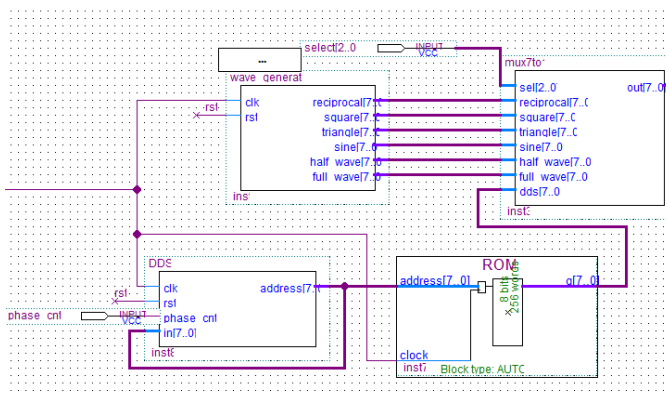


Fig. 7 Verilog description of whole waveform generator

We didn't set this as top module. Thus synthesis summary doesn't exist.

C. Modelsin Results for all waveforms

 


Fig. 7 Simulation of all waveforms

II. DIGITAL TO ANALOG CONVERSION USING PWM

This module convert digital waves to analog.

A. Code of DAC

```

1 module DAC(input clk, rst, input [7:0] wave, output reg pulse);
2     reg[7:0] count = 8'd0;
3
4     always @(posedge clk)
5     begin
6         if (rst)
7             count = 8'd0;
8         else
9             count = count + 8'd1;
10    end
11
12    always @(count)
13    begin
14        pulse = (count < wave) ? 1'b1 : 1'b0;
15    end
16 endmodule
17

```

Fig. 8 Verilog description of DAC model

B. Simulation

 


Fig. 9 Simulation of DAC module

C. Program to FPGA

We add all modules to Quartus and synthesize them. Connected modules together and programmed this top module to FPGA.

 


Fig. 10 reciprocal wave

 


Fig. 13 sine wave

 


Fig. 11 square wave

 


Fig. 14 full wave

 


Fig. 12 triangle wave



Fig. 15 half wave

 


Fig. 16 sine wave with freq 110



Fig. 17 sine wave with freq 111

 


Fig. 18 sine wave with ampliude 10 that half domain

III. FREQUENCY SELECTOR

A. Test and Simulation

1.Frequency Selector

In fig.19 freq = $10^9/5200 = 192$ KHz

 


Fig. 19 sw = 101

In fig.20 freq = $10^9/2700 = 370$ KHz

 


Fig. 20 sw = 110

In fig.21 freq = $10^9/80 = 12$ MHz

 


Fig. 21 sw = 111

2. DDS

We set phase control to 1, 5 and 10

 


Fig. 22 waveform with different phase control of DDS

IV. AMPLITUDE SELECTOR

A. Codes

```
1 module amplitud_Selector(input [1:0] select, input [7:0] in, output [7:0] out);
2   assign out = in >> select;
3 endmodule
```

Fig. 22 Verilog description of amlitude selector

V. TOTAL DESIGN

We import Verilog description to quartus and create some modules like ROM by magic wizards. Then connect all these modules. Compiled it and assigned pins.

A. RTL Design

 


Fig. 25 Block diagram of whole function generator

B. Pin Planner

To	Direction	Location	I/O Bank	VREF Group	Fitter Location
clk	Input	PIN_L1	2	B2_N1	PIN_L1
divison[1]	Input	PIN_U11	8	B8_N0	PIN_U11
divison[0]	Input	PIN_U12	8	B8_N0	PIN_U12
out_pwm	Output	PIN_A13	4	B4_N1	PIN_A13
phase_cnt	Input	PIN_L21	5	B5_N1	PIN_L21
rst	Input	PIN_L22	5	B5_N1	PIN_L22
select[2]	Input	PIN_L2	2	B2_N1	PIN_L2
select[1]	Input	PIN_M1	1	B1_N0	PIN_M1
select[0]	Input	PIN_M2	1	B1_N0	PIN_M2
SW[2]	Input	PIN_W12	7	B7_N1	PIN_W12
SW[1]	Input	PIN_V12	7	B7_N1	PIN_V12
SW[0]	Input	PIN_M22	6	B6_N0	PIN_M22
wave[7]	Output				PIN_A15
wave[6]	Output				PIN_H12
wave[5]	Output				PIN_G12
wave[4]	Output				PIN_F12
wave[3]	Output				PIN_B14
wave[2]	Output				PIN_B13
wave[1]	Output				PIN_C13
wave[0]	Output				PIN_A14

```

1
2 module amp_TB();
3
4 reg clk = 1'b0, rst = 1'b1;
5 wire [7:0] wave, out;
6 reg [1:0] sel = 2'b00;
7
8 sine_wave sine(clk, rst, wave);
9
10 amplitud_Selector as(sel, wave, out);
11
12 initial
13 begin
14     repeat(7000)
15         #10 clk = ~clk;
16     end
17
18 initial begin
19     #10 rst = 1'b0;
20     #(2048 * 10) sel = 2'b01;
21     #(2048 * 10) sel = 2'b10;
22     #(2048 * 10) sel = 2'b11;
23 end
24
25 endmodule

```

Fig. 23 Testbench of amplitude selector

B. Test and Simulation

It is obvious that by increasing phase of amplitude domain of wave decreases.

 


Fig. 24 Testbench of amplitude selector